

## Experiment # 2: Operational Amplifier Characteristics

### Objective:

To measure some of the most important parameters at the basis of op amp limitations: the input pin currents  $I_P$  and  $I_N$ , the input offset voltage  $V_{OS}$ , the common mode and power supply rejection ratios  $CMRR$  and  $PSRR$ , the open loop DC gain  $A_{OL0}$ , the open loop bandwidth  $f_b$ , the transition frequency  $f_t$ , the small signal rise time  $t_R$ , the slew rate  $SR$ , and the upper and lower output saturation limits  $V_{OH}$  and  $V_{OL}$ . To assess the faithfulness of the 741 macromodel available in PSpice.

### Components:

2 × 741C op amps, a 10-k $\Omega$  potentiometer, 3 × 0.1- $\mu$ F capacitors, and miscellaneous resistors: 2 × 100  $\Omega$ , 2 × 10.0 k $\Omega$ , 6 × 100 k $\Omega$ , and 2 × 1.0 M $\Omega$  (all 1%, ¼ W).

### Instrumentation:

A dual  $\pm 15$ -V regulated power supply, a signal generator (sinewave and squarewave), a digital multimeter, and a dual-trace oscilloscope.

### References:

1. Sedra, Adel S., and Smith, Kenneth C., *Microelectronics*, 4<sup>th</sup> Ed, Oxford University Press, 1997.
2. Roberts, Gordon W., and Sedra, Adel S., *SPICE*, 2<sup>nd</sup> Ed., Oxford University Press, 1997.

### Theoretical Background:

Ideally, an op amp has infinite open loop gain regardless of frequency, it draws zero currents at its input pins, and it can provide any voltage or current at its output pin.

In a practical op amp, the open loop gain is not only finite, but it rolls off with frequency. Moreover, the input pins draw tiny currents  $I_P$  and  $I_N$ , where the labels  $P$  and  $N$  denote, respectively, the *non-inverting* and the *inverting* input pins. If we tie the input pins together so that  $v_N = v_P$ , we expect the output  $v_O$  to be zero. In practice  $v_O$  will be different from zero, and if we wish to drive it to zero, a tiny corrective voltage must be applied between the input pins, called the *input offset voltage*  $V_{OS}$ . The parameters  $I_P$ ,  $I_N$ , and  $V_{OS}$  are referred to as *DC imperfections*.

The mean of the two input pin currents is called the *input bias current*  $I_B$ , and their difference is the *input offset current*  $I_{OS}$ , or


$$I_B = (\frac{1}{2})(I_P + I_N) \qquad I_{OS} = I_P - I_N \qquad (1)$$

The data sheets of the popular 741C op amp report the following typical (maximum) room temperature values:

$I_B = 80$  nA (500 nA),  $I_{OS} = 20$  nA (200 nA), and  $V_{OS} = 2.0$  mV (6.0 mV). Note that  $I_{OS}$  and  $V_{OS}$  may be positive or negative, depending on the direction of imbalance.

At low frequencies the open loop gain  $A_{OL}$ , though not infinite, is still fairly large. This gain is aptly called the *DC gain* and is denoted as  $A_{OL0}$ . For the 741C op amp,  $A_{OL0} = 200,000$  V/V typical, 50,000 V/V minimum. An op amp provides this high gain only up to some frequency called the *open loop gain bandwidth*  $f_b$ , after which gain rolls with frequency until a frequency  $f_t$  is reached at which gain becomes unity. Above  $f_t$  gain is less than unity; hence,  $f_t$  is called the *transition frequency*. The 741C op amp typically has  $f_b \cong 5$  Hz and  $f_t \cong 1$  MHz. For most op amps, including the 741 type, gain rolls off at a constant rate of  $-20$  dB/dec, indicating that the open loop gain  $A_{OL}(jf)$  can be expressed mathematically as

$$A_{OL}(jf) = \frac{A_{OL0}}{1 + jf / f_b} \qquad (2)$$

 

**Fig. 1** - Noninverting Op-Amp configuration.

For the 741C op amp,  $A_{OL}(jf) = 200,000/[1 + jf/(5 \text{ Hz})]$  V/V. The *gain bandwidth product* is defined as  $GBP = |A_{OL}| \times f$ . For an op amp with a gain rolloff of  $-20 \text{ dB/dec}$ , this product is constant for  $f \gg f_b$ , namely,  $GBP = f_t$ .

The AC responses of op amps can readily be visualized via PSpice using suitable op amp models called *macromodels*. The file `Eval.lib` that comes with the student version of PSpice contains a 741 macromodel that is invoked via a command of the type


```
XOA vP vN VCC VEE vO ua741
```

Where `vP`, `vN`, `VCC`, `VEE`, and `vO` denote the nodes corresponding to the noninverting input, inverting input, positive supply, negative supply, and output. The following PSpice code is used to display the open loop frequency response of the 741 macromodel, as well as the closed loop frequency response of the non-inverting configuration of Fig. 1 for the case  $R_1 = 100 \, \Omega$  and  $R_2 = 100 \text{ k}\Omega$ , or  $\beta = R_1/(R_1 + R_2) = 1/1001 \text{ V/V}$ . The statement `.lib eval.lib` tells PSpice where to look for the 741 macromodel.

```
741 Frequency Response
.lib eval.lib
VCC 7 0 dc 15V
VEE 4 0 dc -15V
Vi 3 0 ac 1mV
Ri 3 0 1k
R1 0 2 100
R2 2 6 100k
XOA 3 2 7 4 6 ua741
.ac dec 10 1Hz 10megHz
.probe
.end
```

The open loop and closed loop response are shown in Fig. 2.

If we operate a constant GBP Op-amp in the negative feedback mode with a constant feedback factor  $\beta$ , its

 

**Fig. 2** – Open loop and closed loop response of the noninverting Op-amp configuration.

response to a sufficiently small step is an exponential transient characterized by the time constant  $\tau = 1/2\pi\beta f_i$ . The amount of time it takes for this transient to swing from 10% to 90% of its final value is called the *rise time*  $t_R$ . It is readily seen that  $t_R = \tau \ln 9 = 0.35/\beta f_i$ . For instance, a 741C op amp connected as a voltage follower ( $\beta = 1$ ) has  $t_R = 0.35/f_i = 350$  ns. If the amplitude of the input step is gradually increased, a point is reached at which the output becomes slew rate limited, and the initial portion of the transient is a *ramp*. The slope of this ramp is called the *slew rate* ( $SR$ ). For the 741C op amp,  $SR \cong 0.5$  V/ $\mu$ s.


The following PSpice code is used to display the pulse response of the 741 macromodel for the noninverting configuration of Fig. 1 with  $R_1 = 10$  k $\Omega$  and  $R_2 = 100$  k $\Omega$ , or  $\beta = R_1/(R_1 + R_2) = 1/11$  V/V.

```
741 Pulse Response (Small-Signal)
.lib eval.lib
VCC 7 0 dc 15V
VEE 4 0 dc -15V
vI 3 0 pulse (0 5mV 10ns 10ns 10ns 10us 20us)
Ri 3 0 1k
R1 0 2 10k
R2 2 6 100k
XOA 3 2 7 4 6 ua741
.tran 10ns 30us UIC
.probe
.end
```


As shown in Figure 3, the small signal pulse response consists of exponential transients, just like in the case of an ordinary RC network of the type investigated in ENGR 206. However, changing the parameters as in the following PSpice code,

```
741 Pulse Response (Large-Signal)
.lib eval.lib
VCC 7 0 dc 15V
VEE 4 0 dc -15V
Vi 3 0 pulse (0 1V 100ns 100ns 100ns 50us 100us)
Ri 3 0 1k
R1 0 2 10k
R2 2 6 100k
XOA 3 2 7 4 6 ua741
.tran 100ns 120us UIC
.probe
.end
```

results in the large signal pulse response shown in Fig. 4, characterized by slew rate limited ramps.

 

**Fig. 3** – Small signal pulse response with exponential transients.

 

**Fig. 4** – Large signal pulse response.

### Experimental Setup:

Most measurements shall be performed using the circuits of Figs. 5 and 6, which each lab group should assemble simultaneously in separate areas of the protoboard before coming to the lab. This will allow using the allotted lab time efficiently, primarily to perform the required measurements and observations. Please refer to Appendix 2 for useful tips on how to construct op amp circuits. In particular, use two 0.1- $\mu$ F capacitors to bypass the  $\pm 15$ -V power supplies, and always turn off power before making any changes in a circuit. Failure to do so may destroy the op amp, indicating that all measurements performed up to that point will have to be repeated!

Henceforth, steps shall be identified by letters as follows: **C** for calculations, **M** for measurements, and **S** for SPICE simulation. Moreover, each measured value should be expressed in the form  $X \pm \Delta X$  (e.g.  $V_{OS} = 1.5 \text{ mV} \pm 0.1 \text{ mV}$ ), where  $\Delta X$  represents the estimated uncertainty of your measurement, something you have to figure out based on your learning in ENGR 300.

### DC Parameters:


In the circuit of Fig.5, the op amp at the left is the *device under test* (DUT), and the op amp at the right provides a servo loop to force the output of the DUT near 0 V and all possible test conditions. Also, note that to simplify inventory, we implement the 50.0-k $\Omega$  resistance by connecting two 100-k $\Omega$  in parallel.

**C1:** Show that with the given component values, the circuit of Fig. 5 yields

$$v_2 = 500(R_p I_P - R_n I_N - V_{OS} - v_1 / A_{OL}) \quad (3)$$

where  $I_P$  and  $I_N$  are the input pin currents of the DUT, assumed to be flowing into the DUT, and  $V_{OS}$  and  $A_{OL}$  are the input offset voltage and open loop gain of the DUT. The switches shown are ordinary wires that are used to selectively short out the corresponding resistors and thus force one or more of the terms in Eq. (3) to vanish.

**M1:** With both  $SW_1$  and  $SW_2$  closed and  $v_1 = 0 \text{ V}$  (ground), measure  $v_2$  with the digital voltmeter (DVM). Hence, use Eq. (3) to find  $V_{OS}$ .

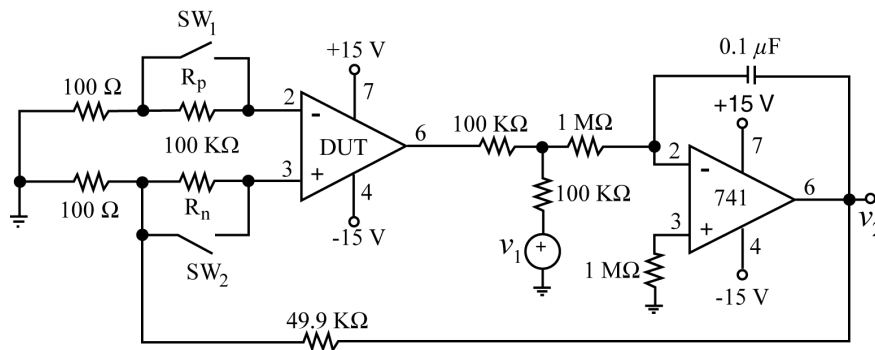

**Fig. 5** – Experimental setup to measure DC parameters.

**M2:** With  $SW_1$  closed,  $SW_2$  open, and  $v_1 = 0$  V (ground), measure  $v_2$  with the (DVM). Hence, use Eq. (3), along with the result of Step M1, to find  $I_P$ .

**M3:** With  $SW_1$  open,  $SW_2$  closed, and  $v_1 = 0$  V (ground), measure  $v_2$  with the (DVM). Hence, use Eq. (3), along with the result of Step M1, to find  $I_N$ .

**M4:** With both  $SW_1$  and  $SW_2$  closed and  $v_1 = 15$  V (use the +15-V supply), measure  $v_2$  with the (DVM). Hence, use Eq. (3), along with the result of Step M1, to find  $A_{OL0}$ .

**C5:** Using Eq. (1), calculate  $I_B$  and  $I_{OS}$ . Hence, compare your values of  $I_B$ ,  $I_{OS}$ ,  $V_{OS}$ , and  $A_{OL0}$  with those given in the data sheets. Comment.

**M6:** With both  $SW_1$  and  $SW_2$  closed and  $v_1 = 0$  V (ground), lower the positive supply  $V_{CC}$  from +15 V to +10 V while keeping  $V_{EE} = -15$  V. Measure with the DVM the resulting variation in  $v_2$ , and hence calculate the corresponding change  $\Delta V_{OS}$ . Finally, calculate the *positive power supply rejection ratio* as  $PSRR_p = 20 \ln |\Delta V_{CC} / \Delta V_{OS}|$ .

**M7:** Repeat Step M5, except that now you keep  $V_{CC} = +15$  V and change  $V_{EE}$  from -15 V to -10 V. The result is now the *negative power supply rejection ratio* as  $PSRR_n = 20 \ln |\Delta V_{EE} / \Delta V_{OS}|$ . Compare the two  $PSRR$ s, comment.

### Offset Nulling:


For the next set of measurements we use the circuit of Fig. 6 with  $R_1 = R_4 = 100 \Omega$  and  $R_2 = R_3 = 100 \text{ k}\Omega$ . Given the high closed loop gain (1001 V/V), the input  $v_I$  must be kept suitably small to avoid saturation effects at the output, so we use an input voltage divider, as shown. Since the resistances of the divider are the same as those in the feedback network, the overall low frequency gain from  $v_S$  to  $v_O$  is nominally unity. Initially, the 10-k $\Omega$  potentiometer is left out of the circuit.

**C8:** Ignoring the 10-k $\Omega$  pot in the circuit of Fig. 6, use the results of your previous measurements to predict the value of  $v_O$  with  $v_S = 0$  V (ground). Next, apply power but without connecting the 10-k $\Omega$  potentiometer yet, and measure  $v_O$  with the DVM. How does it compare with the predicted value? Comment.

Next, turn off power, connect the 10-k $\Omega$  pot in the manner shown, reapply power, and adjust its wiper until  $v_O$  comes as close as possible to 0 V. The purpose of the pot is to deliberately imbalance the internal circuitry of the op amp so as to make it possible for us to drive  $v_O$  to zero. This action is referred to as *internal offset nulling*. Once the pot has been adjusted, it should not be touched again.

### Frequency Response:

For this response, use still the circuit of Fig. 6 with  $R_1 = R_4 = 100 \Omega$  and  $R_2 = R_3 = 100 \text{ k}\Omega$ , and monitor  $v_S$  and  $v_O$  with Ch. 1 and Ch. 2 of the oscilloscope (both channels on DC, Trigger from Ch. 1, Chop Mode; make sure you know where the 0-V baselines of your traces are!) Adjust the signal generator so that  $v_S$  is a sinusoidal wave with a

 

**Fig. 6** - Circuit used for offset nulling.

1-V amplitude (2-V peak-to-peak) and 0-V DC offset.

**M9:** Starting at low input frequencies, increase frequency until the amplitude of  $v_O$  drops to 0.707 of its low frequency value. This frequency is the  $-3$ -dB frequency  $f_{-3dB}$ , which is related to the transition frequency  $f_t$  as  $f_{-3dB} = \beta f_t$ .

**M10:** Measure the amplitude of  $v_O$  also at  $10f_{-3dB}$  and  $100f_{-3dB}$ , and verify the constancy of the  $GBP$ . Hence, estimate  $f_t$ .

**C11:** Using the value of  $A_{OL0}$  obtained in step M4, estimate  $f_b$ . Hence, sketch the magnitude Bode Plots of both the open loop and closed loop responses of the circuit of Fig. 7.

**S12:** Rerun the 741 Frequency Response PSpice program above, and use the cursor facility to determine  $A_{OL0}$ ,  $f_b$ ,  $f_t$ , and  $f_{-3dB}$ . Hence, compare with your measured values and comment on the quality of the 741 PSpice macromodel in the frequency domain.

### Small-Signal Transient Response:

For this response use still the circuit of Fig. 6, but with  $R_1 = R_4 = 10 \text{ k}\Omega$  and  $R_2 = R_3 = 100 \text{ k}\Omega$  (make sure you turn power off as you change  $R_1$  and  $R_4$  from the previous step). Also, adjust the signal generator so that  $v_S$  is a squarewave alternating between 0 V and +55 mV.

**M13:** Adjust the input frequency so that the waveforms appear somewhat as in Fig. 3. Hence, using the techniques of ENGR 206, measure the rise time  $t_R$ . How does the measured value compare with the expected value  $t_R = 0.35/\beta f_t$ ? Comment.

**S14:** Rerun the 741 Pulse Response (Small-Signal) program above, and use the cursor facility to determine  $t_R$ . Hence, compare with your measured value and comment on the quality of the 741 PSpice macromodel in the time domain.

### Large-Signal Response:

For this response, use still the circuit of Fig. 6, but with  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = R_3 = 100 \text{ k}\Omega$ , and  $R_4$  removed from the circuit. Then, rise the input pulse amplitude to 1 V.

**M15:** Adjust the input frequency so that the waveforms appear somewhat as in Fig. 4. Hence, determine the slopes of the two ramps, in V/ $\mu$ s. How do they compare with the data sheet  $SR$  value for the 741C?

**M16:** Adjust  $v_S$  so that it is a 1-kHz sinewave alternating between about  $-1 \text{ V}$  and  $+1 \text{ V}$ . Then, gradually rise the amplitude of  $v_S$  until  $v_O$  clips. Measure on the oscilloscope the upper and lower saturation limits  $V_{OH}$  and  $V_{OL}$ . Are they symmetric? Different? Justify.

**M17:** Reduce  $v_S$  until the peaks of  $v_O$  are just a bit less than the saturation limits, say, 0.5-V less. Then, rise the input frequency until  $v_O$  just begins to distort near its zero crossings. This distortion is due to slew rate limiting, and the frequency corresponding to the onset of distortion is the *full power bandwidth (FPB)*. Compare the measured value of  $FPB$  with the predicted value  $FPB = SR/2\pi V_{om}$ , where  $V_{om}$  is the peak amplitude of  $v_O$ ; comment.

**M18:** Reduce  $v_S$  to half its value of Step M17, and find the new input frequency at which  $v_O$  just begins to distort near its zero crossings. Again, compare with the predicted value  $FPB = SR/2\pi V_{om}$ ; comment.

### The Voltage Follower

For this part, use still the circuit of Fig. 6, but with  $R_2 = R_3 = 10 \text{ k}\Omega$ , and  $R_1$  and  $R_4$  removed from the circuit, so that we now have a voltage follower.


**MS19:** Measure the frequency response, as well as the small signal and large signal pulse responses; simulate all three responses with PSpice; compare simulations and measurements; comment.

### The Difference Amplifier and the CMRR:

For this part, use the circuit of Fig. 7, which is similar to that of Fig. 6, except that  $R_1$  and  $R_2$  are tied together and driven with a common signal  $v_S$ . For the variable resistance, use the 10-k $\Omega$  pot you used for offset nulling. Initially, assemble the circuit without the 2-M $\Omega$  resistance, and with the wiper all the way to the left, so that the variable resistance is 0  $\Omega$ . Make sure power is off as you assemble your circuit! Also, adjust  $v_S$  so that it is a 100-Hz sinewave with peak amplitude  $V_{im} = 5$  V and 0-V DC offset.

**M20:** With the 2-M $\Omega$  resistor initially disconnected and the wiper all the way to the left, measure the peak amplitude  $V_{om}$  of  $v_O$ . Then, calculate the *common mode* voltage gain  $A_{cm} = V_{om}/V_{im}$ , and hence, the *common mode rejection ratio*  $CMRR = 20 \log |A_{dm}/A_{cm}|$ , where  $A_{dm} = R_2/R_1$  is the *differential mode* gain.

**M21:** Turn power off, insert the 2-M $\Omega$  resistor (implement it by recycling the two 1-M $\Omega$  resistors of Fig. 5 and connect them in series), reapply power, and vary the wiper until  $v_O$  is minimized. This, in turn, maximizes the *CMRR* of the circuit. What is its new value, in dB?

 

**Fig. 7** - Circuit to investigate the difference amplifier and the CMRR.


## APPENDIX 2: TIPS ON OP AMP CIRCUIT LAYOUT AND PRECAUTIONS

Unless otherwise specified, op amps shall be powered from  $V_{CC} = +15\text{V}$  and  $V_{EE} = -15\text{V}$ . Due to their extremely high gains, op amps are prone to oscillation. To prevent unwanted oscillations, you should systematically abide by the following rules:

1. Bypass the supply leads to the op amp towards ground by means of two good RF capacitors, such as 0.1-  $\mu\text{F}$  disc ceramic or 1.0 $\mu\text{F}$  tantalum capacitors.
2. Use minimum-length layouts. This applies especially to the op amp's inverting input lead in negative-feedback configurations.
3. If you need to observe the voltage at any one of the op amp's critical pins, particularly the inverting- input pin, by means of the oscilloscope or the DMM, avoid connecting the instrument's lead directly to the op amp's critical pin. Always place a series resistor, say 10 k $\Omega$ , between the two.


IC op amps are fairly delicate devices; as such they can easily be destroyed, unless suitable precautions are taken, as follows:

4. Whenever you need to make a circuit change, turn the power supplies off. After making your change, check once more for possible wiring errors before reapplying power.
5. To prevent damaging the op amp input stage, make sure the voltage you apply to either input terminal never exceeds  $+V_{CC}$  and never goes below  $-V_{EE}$ ; this happens, for instance, if the power supplies are turned off while the input signal generator is still on. To avoid damaging the input stage, it is a good idea to use a series resistance, say, 10 k $\Omega$ , between the signal generator and the input pin.
6. Don't connect anything to the op amp pins that are not in use.

 

**Fig. A2.1** - Pinout for the 741 op amp, and power-supply interconnection for the inverting configuration.



 

**Fig. A2.2** -Recommended conventions and circuit layout for op amp circuits. The example refers to a  $\mu A741$  connected as an inverting amplifier, but the features of this example should be applied to other circuits and op amps as well.