

## Experiment # 5: MOSFET Characteristics and Applications

### Objective:

To characterize *n-channel* and *p-channel enhancement MOSFETs*. To investigate basic *MOSFET amplifiers*. To compare *measured* and *simulated* MOSFET circuits.

### Components:

2 × CD4007UB MOSFET Arrays, 2 × 0.1 μF capacitors, 1 × 10 kΩ potentiometer, and miscellaneous resistors: 1 × 100 Ω, 4 × 10 kΩ, and 1 × 1 MΩ (all 1%, ¼ W).

### Instrumentation:

A bench power supply, a signal generator (sine/triangle wave), a digital multimeter, and a dual-trace oscilloscope.

### References:

1. Sedra, Adel S., and Smith, Kenneth C., *Microelectronics*, 4<sup>th</sup> Ed, Oxford University Press, 1997.
2. Roberts, Gordon W., and Sedra, Adel S., *SPICE*, 2<sup>nd</sup> Ed., Oxford University Press, 1997.

### Theoretical Background:

When an *n-channel MOSFET* (*nMOSFET*) is biased in the *active region*, also called *pinch-off* or *saturation region*, and defined by the conditions

$$v_{GS} \geq V_{in} \quad (1a)$$

$$v_{DS} \geq v_{GS} - V_{in} \quad (1b)$$

its drain current  $i_D$  is related to the applied gate-source voltage  $v_{GS}$  and the operating drain-source voltage  $v_{DS}$  as

$$i_D = (k_n/2) \times (v_{GS} - V_{in})^2 \times (1 + \lambda_n v_{DS}) \quad (2)$$

where  $k_n$ , a scale factor whose units are A/V<sup>2</sup>, is called the *device transconductance parameter*;  $V_{in}$  is called the *threshold voltage*; and  $\lambda_n$ , whose dimensions are V<sup>-1</sup>, is called the *channel length modulation parameter* ( $\lambda_n$  is the reciprocal of the Early voltage  $V_A$  of BJTs, or  $\lambda_n = 1/V_{An}$ ). For low power MOSFETs,  $k_n$  is typically in the range of 10<sup>1</sup> to 10<sup>2</sup> μA/V<sup>2</sup>,  $V_{in}$  is in the range of a few V, and  $\lambda_n$  is on the order of 10<sup>-1</sup> to 10<sup>-2</sup> V<sup>-1</sup>. A given pair of values  $I_D$  and  $V_{DS}$  in the  $i_D$ - $v_{DS}$  plane define a unique point called the *operating point*  $Q(I_D, V_{DS})$  of the MOSFET.

The device transconductance parameter  $k_n$  depends on device geometry as

$$k_n = k' \left( \frac{W_n}{L_n} \right) \quad (3)$$

where  $k'$ , also in A/V<sup>2</sup>, is called the *process transconductance parameter*; and  $W_n$  and  $L_n$ , both in μm, are the channel *width* and channel *length* of the MOSFET.

If  $V_{in} > 0$ , the *nMOSFET* is said to be of the *enhancement type*; if  $V_{in} < 0$ , it is said to be of the *depletion type*. The threshold voltage  $V_{in}$  depends on the body bias voltage  $V_{SB}$  as

$$V_{in} = V_{in0} + \gamma_n \left( \sqrt{2\phi_{fn} + V_{SB}} - \sqrt{2\phi_{fn}} \right) \quad (4)$$

where  $V_{in0}$  is the threshold voltage in the absence of any body bias ( $V_{SB} = 0$ );  $\gamma_n$ , in V<sup>1/2</sup>, is called the *body effect coefficient*, and is typically 0.5 V<sup>1/2</sup>; finally,  $\phi_{fn}$  is the *equilibrium electrostatic potential* of the body, typically 0.3 V.

Note that for  $n$ MOSFETs the *body*, or *substrate*, must *never* be biased *more positive* than the source, that is, we must always have  $V_{SB} \geq 0$ .

Similar considerations hold for  $p$ -channel MOSFETs ( $p$ MOSFETs), provided we *reverse* all current directions and voltage polarities. Thus, while in an  $n$ MOSFET  $i_D$  flows *into* and  $i_S$  flows *out* of the device, in a  $p$ MOSFET  $i_D$  flows *out* and  $i_S$  flows *into* the device. Moreover, the active region conditions of Eq. (1) become, for a  $p$ MOSFET,

$$v_{SG} \geq -V_{tp} \quad (5a)$$

$$v_{SD} \geq v_{SG} + V_{tp} \quad (5b)$$

Similarly, Eq. (2) is rephrased as

$$i_D = \left( \frac{k_p}{2} \right) \times (v_{SG} + V_{tp})^2 \times (1 + \lambda_p v_{SD}) \quad (6)$$

where  $k_p = k'(W_p/L_p)$  is the device transconductance parameter. If  $V_{tp} < 0$ , the  $p$ MOSFET is said to be of the *enhancement type*; if  $V_{tp} > 0$ , it is said to be of the *depletion type*. Equation (3) holds for all MOSFETs, regardless of the channel type, while Eq. (4) becomes, for a  $p$ MOSFET,

$$V_{tp} = V_{tp0} - \gamma_p \left( \sqrt{-2\phi_{fp} + V_{BS}} - \sqrt{-2\phi_{fp}} \right) \quad (7)$$

Where now  $\phi_{fp}$  is typically -0.3 V. Note that for  $p$ MOSFETs the *body*, or *substrate*, must *never* be biased *more negative* than the source, that is, we must always have  $V_{BS} \geq 0$ .


MOSFET circuits are readily simulated using PSpice. To this end, we must first create a MOSFET model which, for the case of an  $n$ -channel device called `our_nMOSFET` takes on the form

```
.model our_nMOSFET nmos (kp=kval Vto=Vval lambda=lval gamma=gval)
```

where `kval`, `Vval`, `lval`, and `gval` are, respectively, the measured values of  $k'$ ,  $V_{tn0}$ ,  $\lambda_n$ , and  $\gamma_n$ . Then, to invoke a transistor `MXXX`, we use a statement of the type

```
MXXX D G S B our_nMOSFET W=Wval L=Lval
```

where `D`, `G`, `S`, and `B` are the drain, gate, source, and body terminals, in that specific order, and `Wval` and `Lval` are the values of  $W_n$  and  $L_n$ . The following PSpice code uses the circuit of Fig. 1 to display the  $i_D$ - $v_{DS}$  characteristics of an enhancement  $n$ MOSFET called `M1` and having  $W_n = L_n = 10 \mu\text{m}$ ,  $k' = 200 \mu\text{A/V}^2$ ,  $V_{tn0} = 1.5\text{V}$ , and  $\lambda_n = 0.05 \text{V}^{-1}$ :

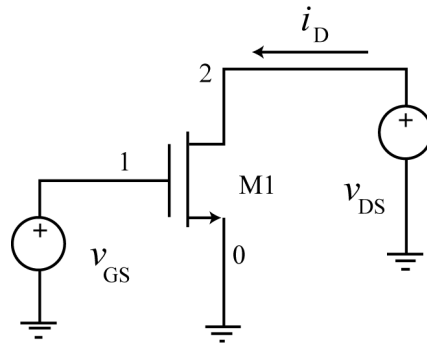

**Fig. 1** - PSpice Circuit to display the  $i$ - $v$  characteristics of a MOSFET.

```

MOSFET Characteristics
vGS 1 0 dc 0V
vDS 2 0 dc 0V
M1 2 1 0 0 our_nMOSFET W=10u L=10u
.model our_nMOSFET nmos (kp=200u Vto=1.5V lambda=0.05)
.dc vDS 0V 10V 100mV vGS 0V 5V 0.5V
.probe
.end

```

The characteristics are shown in Fig. 2.

The following PSpice code is used to simulate the basic CS amplifier of Fig. 3 using the same MOSFET model of above:

```

CS Amplifier
VDD 3 0 dc 10V
vs 1 0 ac 100mV
C1 1 2 0.1uF
RG 2 4 10Meg
RD 3 4 10k
M1 4 2 0 0 our_nMOSFET W=10u L=10u
.model our_nMOSFET nmos (kp=200u Vto=1.5V lambda=0.05)
C2 4 5 1uF
RL 5 0 100k
.ac lin 1 10kHz 10kHz
.print ac Vm(1) Vp(1) Vm(5) Vp(5)
.end

```

After running PSpice, we obtain an output file with the following information:


BIAS SOLUTION:

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(1)	0.0000	(2)	3.7858	(3)	10.0000
NODE	VOLTAGE	NODE	VOLTAGE		
(4)	3.7858	(5)	0.0000		


AC ANALYSIS:

FREQ	VM(1)	VP(1)	VM(5)	VP(5)	1.000E+04	1.000E+00	0.000E+00	3.991E-0100	-1.800E+02

We readily find the gain of this amplifier to be  $v_o/v_s = VM(5)/VM(1) = -0.3991/0.1 = -3.991$  V/V, where the negative sign is implied by the fact that  $VP(5) = -180^\circ$ . You may find it instructive to confirm the above data (both bias and ac) via hand calculations!

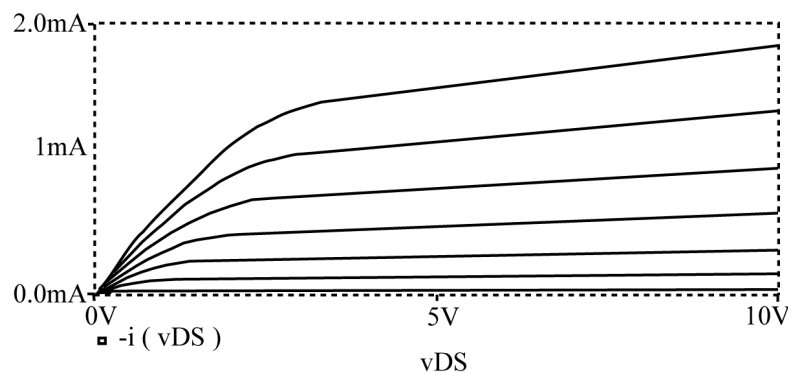

**Fig. 2** - PSpice plot for the MOSFET of Fig. 1.

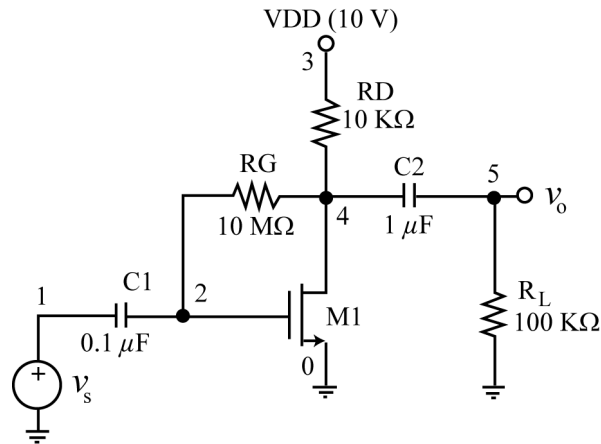

**Fig. 3** - Simple MOSFET amplifier.

### The CD4007UB MOSFET Array:

We shall perform our measurements and experiments using the CD4007UB MOSFET Array. This array consists of three *n*MOSFETs and three *p*MOSFETs, all of the enhancement type, with the interconnections shown in Fig. 4. Note that the body of the *n*MOSFETs (pin 7), which is *p*-type, must always be connected to the *most negative voltage* (MNV) in the circuit; likewise, the body of the *p*MOSFETs (pin 14), which is *n*-type, must always be connected to the *most positive voltage* (MPV) in the circuit. Failure to respect these constraints may invalidate all measurements taken.

### Pinchoff-Region Characteristics:

We shall use the circuits of Figs. 5 and 6 to find  $V_t$  and  $k$ , the circuits of Figs. 7 and 8 to find  $\lambda$ , and the circuits of Figs. 9 and 10 to find  $\gamma$ . In the circuits of Figs. 5 and 6  $v_s$  is a variable DC source which is used along with  $R$  to establish prescribed values of  $i$ . To perform your  $i$  and  $v$  measurements, first configure your digital multimeter (DMM) as an *ammeter in series* between the resistance  $R$  and the drain  $D$  to set  $i$ , then as a *voltmeter in parallel* with the MOSFET to measure  $v$ . In case your ammeter has been put out of service by abuse, you can still use your DMM to perform current measurements as follows: Before inserting  $R$  in the circuit, measure it with the ohmmeter; then insert  $R$ , and while monitoring with the voltmeter the voltage  $v_R$  across  $R$ , adjust  $v_s$  for the desired value of  $i$  (for instance, to obtain  $i = 100 \mu\text{A}$  with  $R = 98 \text{ k}\Omega$ , adjust  $v_s$  until  $v_R = R \times i = 98 \times 0.100 = 9.8 \text{ V}$ ).

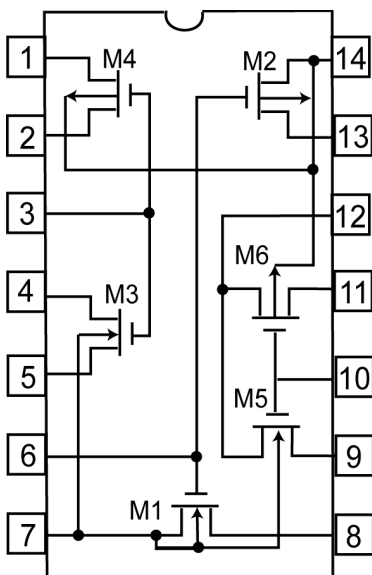


Fig. 4 (a)

**Fig. 4** - CD4007 MOSFET Array.


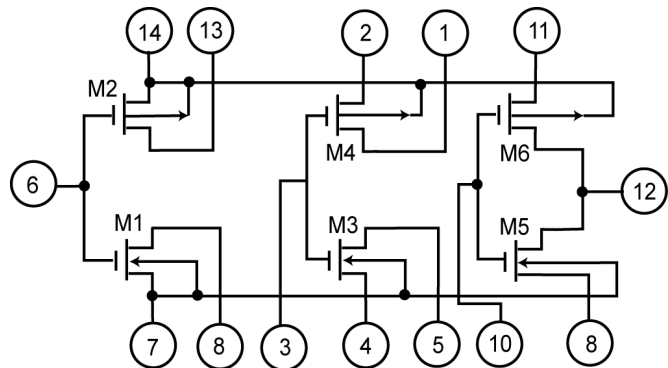



Fig. 4 (b)

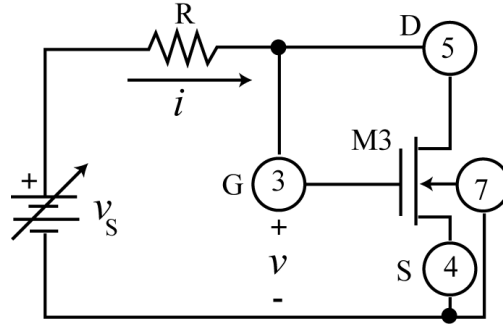

**Fig. 5** - Circuit setup to characterize a *n*MOSFET.


Mark one of your CD4007UB ICs, and as you interconnect parts of it in the circuits below, use short leads and bypass the power supplies with 0.1- $\mu$ F capacitors, as recommended in Appendix A2.

**M1:** For the *n*MOSFET of Fig. 5, measure  $v$  for the following values of  $i$  (shown within parentheses are the corresponding recommended values of  $R$ ):  $i = 0.1$  mA (100 k $\Omega$ ),  $i = 0.4$  mA (20 k $\Omega$ ; use  $2 \times 10$ -k $\Omega$  resistors in series), and  $i = 2$  mA (5.0 k $\Omega$ ; use  $2 \times 10$ -k $\Omega$  resistors in parallel). Then, repeat for the *p*MOSFET of Fig. 6. As usual, all your data should be expressed in the form  $X \pm \Delta X$ .

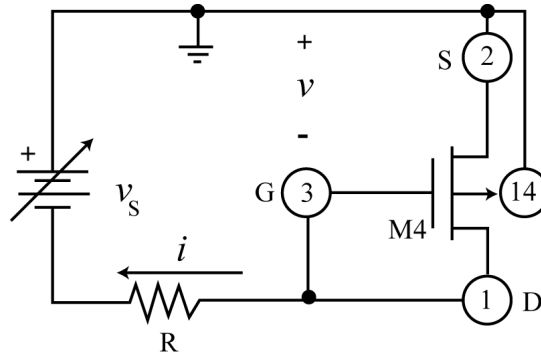

**Fig. 6** - Circuit setup to characterize a *p*MOSFET.

**M2:** For the *n*MOSFET of Fig. 7 adjust the potentiometer until  $V_{DS} = 5$  V (for  $R_D$  use  $2 \times 10$ -k $\Omega$  resistors in parallel). Also, record the value of  $V_{GS}$ , which will be needed in Step M6. Next, turn off power, configure your DMM as a DC ammeter, break the circuit at node *D*, insert the ammeter in series, reapply power and measure  $I_D$  both with  $R_D$  in place as shown, and with  $R_D$  shorted out with a wire. The difference  $\Delta I_D$  between the two readings will be small, so make sure to use as many digits as your ammeter will allow. Note that shorting out  $R_D$  is designed to cause a change  $\Delta V_{DS} = 5$  V. As usual, all your data should be expressed in the form  $X \pm \Delta X$ .

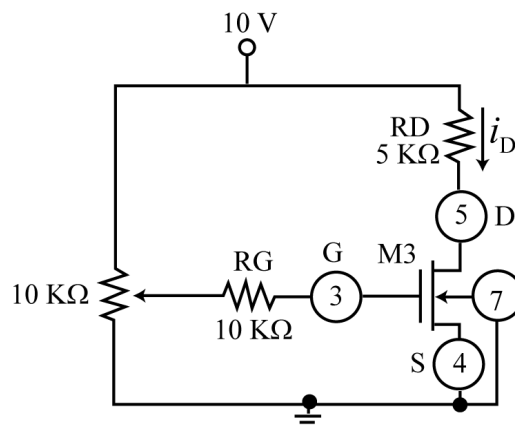

**Fig. 7** - Circuit to determine  $\lambda_n$ .

**M3:** Repeat Step M2 for the *p*MOSFET of Fig. 8, after having adjusted the potentiometer for  $V_{SD} = 5$  V. Record also the value of  $V_{SG}$ , which will be needed in Step M7.

**C4:** Using the *n*MOSFET data of Step M2, find  $r_{on} = \Delta V_{DS} / \Delta I_D$  and, hence,  $\lambda_n = 1/V_{An} = 1/(r_{on}I_D - V_{DS})$ . Likewise, using the *p*MOSFET data of Step M3, find  $r_{op} = \Delta V_{SD} / \Delta I_D$  and, hence,  $\lambda_p = 1/V_{Ap} = 1/(r_{op}I_D - V_{SD})$ .

**C5:** Let us now introduce the quantities

$$x = v \quad y = \sqrt{\frac{i}{1 + \lambda v}}$$

Using the *n*MOSFET set of  $i$  and  $v$  data of Step M1, along with the value of  $\lambda_n$  found in Step C4, calculate the corresponding values of  $y$ , plot them on  $x$ - $y$  graph paper, and draw the best fit straight line; in view of Eq. 2, the intercept of this line with the  $x$ -axis yields  $V_{m0}$ , and its slope yields  $(k_n/2)^{1/2}$ , which allows us in turn to find  $k_n$ . Then repeat the procedure for the *p*MOSFET, keeping in mind that in this case the intercept of the best fit straight line with the  $x$ -axis yields  $-V_{p0}$ , and its slope yields  $(k_p/2)^{1/2}$ , which, in turn, we use to find  $k_p$ .


**MC6:** Turn power off in the circuit of Fig. 7, lift the *p*-body (pin 7) off ground, and return it to a  $-5$ -V supply via a protective  $10$ -k $\Omega$  series resistor as shown in Fig. 9. Reapply power, adjust the potentiometer until you get again  $V_{DS} = 5$  V, and record the new value of  $V_{GS}$ . Then, apply Eq. (4) to find

$$\gamma_n = \frac{\Delta V_{GS}}{\sqrt{2\phi_{fn} + V_{SB}} - \sqrt{2\phi_{fn}}}$$


where  $\Delta V_{GS}$  is the difference between the current value of  $V_{GS}$  and that found in Step M2, and  $\phi_{fn} = 0.3$  V.

**MC7:** Turn power off in the circuit of Fig. 9, lift the *n*-body (pin 14) off ground, and return it to a  $+5$ -V supply via a protective  $10$ -k $\Omega$  series resistor as shown in Fig. 10. Reapply power, adjust the potentiometer until you get again  $V_{SD} = 5$  V, and record the new value of  $V_{SG}$ . Then, apply Eq. (7) to find

$$\gamma_p = \frac{\Delta V_{SG}}{\sqrt{-2\phi_{fp} + V_{BS}} - \sqrt{-2\phi_{fp}}}$$

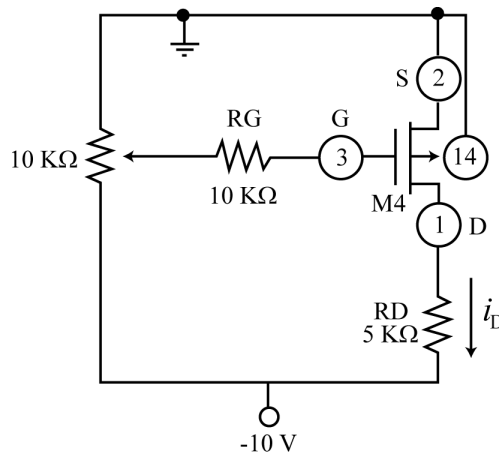

**Fig. 8** - Circuit to determine  $\lambda_p$ .

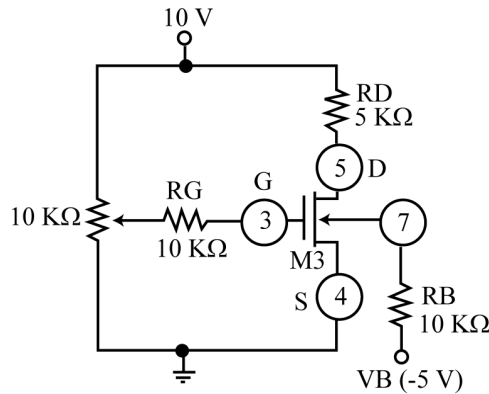

**Fig. 9** - Circuit to determine  $\gamma_n$ .

where  $\Delta V_{SG}$  is the difference between the current value of  $V_{SG}$  and that recording Step M3, and  $\phi_{fn} = -0.3$  V. Summarize your numerical findings for  $k_n$ ,  $V_{th0}$ ,  $\lambda_n$ ,  $\gamma_n$ , and  $k_p$ ,  $V_{th0}$ ,  $\lambda_p$ ,  $\gamma_p$ , and express all data in the form  $X \pm \Delta X$ .

**S8:** Use PSpice to display the  $i_D$ - $v_{DS}$  characteristics of your  $n$ MOSFET, as well as the  $i_D$ - $v_{SD}$  characteristics of your  $p$ MOSFET. Do it both for the case of 0-V and 5-V body bias. Comment on your findings.

### Common-Source Amplifier:

With power off, assemble the circuit of Fig. 11, keeping the leads short and bypassing the power supply with a 0.1  $\mu$ F capacitor.


**C9:** Predict the DC voltage  $V_D$  at the drain terminal in Fig. 11, as well as the small signal gain  $A_v = v_o/v_s$ .

**M10:** While monitoring  $v_s$  with Ch.1 of the oscilloscope (DC mode, Trigger on Ch. 1), adjust the signal generator so that  $v_s$  in Fig. 11 is a 10-kHz sinewave with 0-V DC and 0.5-V peak amplitude. Next, use CH. 2 (DC mode, Chop Mode), to measure the DC voltage at the drain pin; finally, switch Ch. 2 to the AC mode and measure the peak amplitude of  $v_o$ ; hence, find the gain  $A_v = v_o/v_s$  of your amplifier.


**S11:** Simulate the circuit of Fig. 11 using PSpice. For a realistic simulation, you need to create a PSpice model for your specific  $n$ MOSFET sample, using the above measured values of  $k_n$ ,  $V_{th0}$ ,  $\lambda_n$ , and  $\gamma_n$ .

**C12:** Compare the predicted values of Step C9 with the measured values of Step M10 and the simulated values of Step S11; account for any possible discrepancies.

**M13:** Returning to the circuit of Fig. 11, switch Ch. 2 back to the DC mode (make sure you know where your 0-V baseline is on the screen!), change the input generator's waveform to triangular, and rise its amplitude until  $v_o$  distorts both at the top and at the bottom. Justify the two types of distortion in terms of transistor operation.

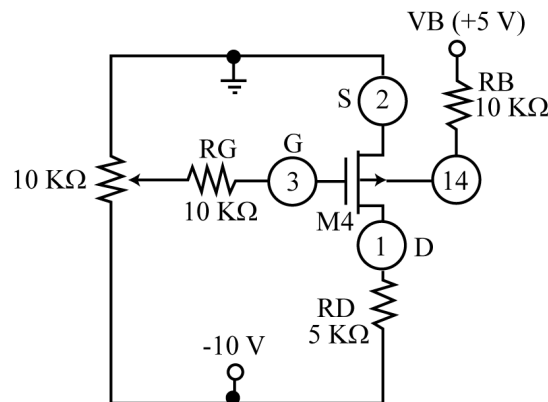

**Fig. 10** - Circuit to determine  $\gamma_p$ .

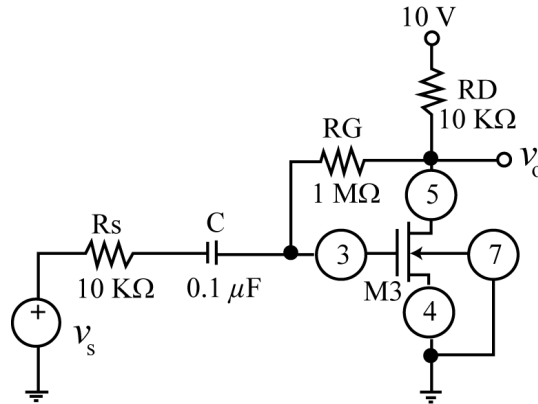

**Fig. 11** - Common-source amplifier.

### Common-Drain Amplifier:

With power off, assemble the circuit of Fig. 12, keeping leads short and using a 0.1-μF power supply bypass capacitor, as usual. Then, adjust the input source so that  $v_s$  is a 10-kHz sinewave with 0-V DC and 2-V of peak-to-peak amplitude.


**CMS14:** In Fig. 12 predict the DC voltage  $V_S$ , as well the small signal gain  $A_v = v_o/v_i$ . Next, measure  $V_S$  and  $A_v$ . Next, find  $V_S$  and  $A_v$  via PSpice. Finally, compare the three sets of values, and account for possible discrepancies.

### CMOS Amplifier:

One of the most popular MOSFET amplifier configurations is the *complementary MOS* (CMOS) cell of Fig. 13, consisting of an *n*MOSFET and a *p*MOSFET with the gates tied together to form the input node, and the drains tied together to form the output node. As you assemble this circuit, keep leads short and use a 0.1-μF power supply bypass capacitor, as usual. Since this stage exhibits a fairly high gain, its input  $v_i$  must be suitably small, so we interpose a voltage divider  $R_1$  and  $R_2$  between the input source and the amplifier to suitably scale down the source. With the resistances shown we have  $v_i \cong v_s/100$ .

**C15:** For the circuit of Fig. 13 predict the DC output voltage  $V_O$  as well as the small signal gain  $A_v = v_o/v_i$ .


**M16:** While monitoring  $v_s$  with Ch.1 of the oscilloscope (DC mode, Trigger from Ch. 1), adjust the input signal generator so that  $v_s$  in Fig. 13 is a 10-kHz sinewave with 0-V DC and 1-V peak amplitude (this makes  $v_i$  a 10-mV peak amplitude sinewave). Next, use CH. 2 (DC mode, Chop Mode), to measure  $V_O$ . Now, switch Ch. 2 to the AC mode and measure the peak amplitude of  $v_o$ ; finally, find the gain  $A_v = v_o/v_i$  of your amplifier.

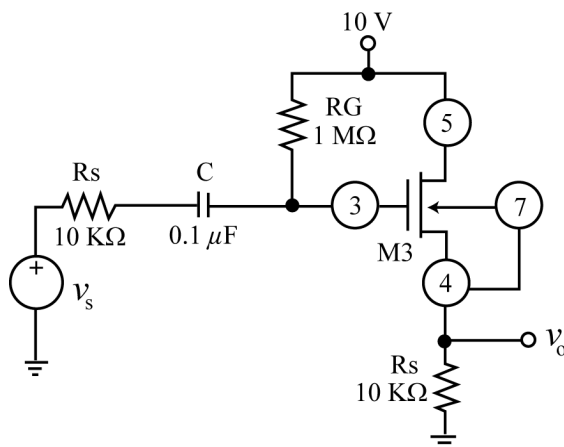

**Fig. 12** - Common-drain amplifier.



**SC17:** Simulate the circuit of Fig. 13 using PSpice; then, compare predicted, measured, and simulated values, and account for any possible discrepancies.

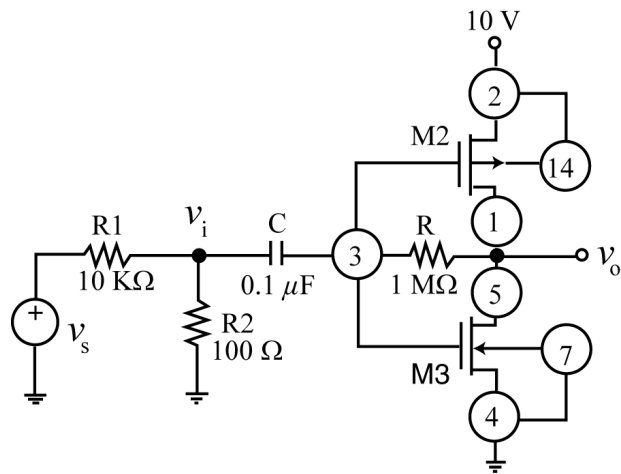

**Fig. 13** – CMOS amplifier.